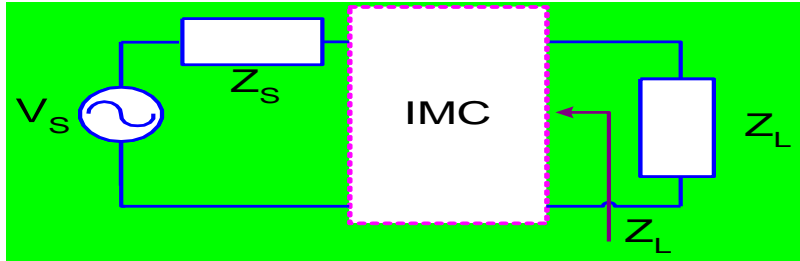


JAWABAN SOAL NO.2

$f=2\text{MHz}$; $Z_s=(10 - j10)\Omega$ dan $Z_L=(20 + j200)\Omega \rightarrow Z_s < Z_L \rightarrow$ **L-kanan HPF**




Untuk mempermudah perhitungan selanjutnya, maka beban Z_L dirubah ke model paralel:

$$Q_s = Q_p = \sqrt{\frac{R_p}{R_s} - 1}$$

$$Q_s = \frac{X_s}{R_s} = \frac{200}{20} = 10$$

$$Q_p = \frac{R_p}{X_p} = 10$$
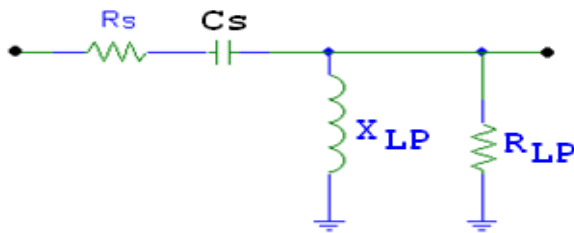
$$R_{LP} = R_s(1 + Q^2) = 2020\Omega; \quad X_{LP} = X_s(1 + 1/Q^2) = 202\Omega$$





a)Metoda Resonansi :

$$X_{rs} = X_s = -10; \text{ dan } 1/X_{rl} = -1/X_{lp} = -1/202; X_{RPL} = -202 \Omega$$

$$C_s = 7,96\text{nF } (-j10\Omega); L_{RS} = 0,796\mu\text{H } (+j10\Omega);$$
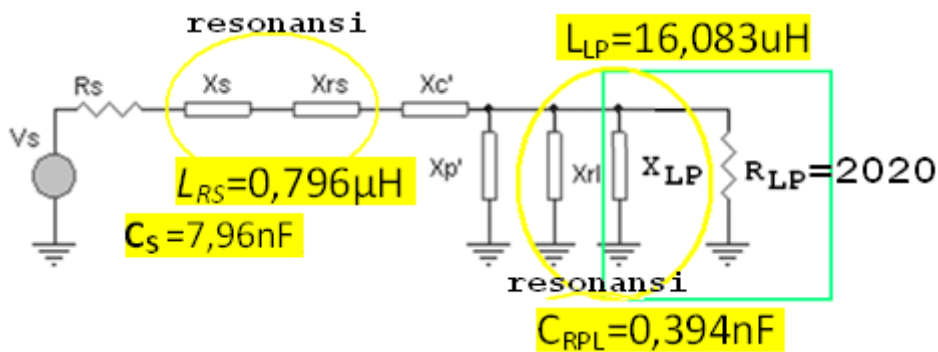
$$L_{LP} = 16,083\mu\text{H } (+j202\Omega); C_{RPL} = 0,394\text{nF } (-j202\Omega);$$



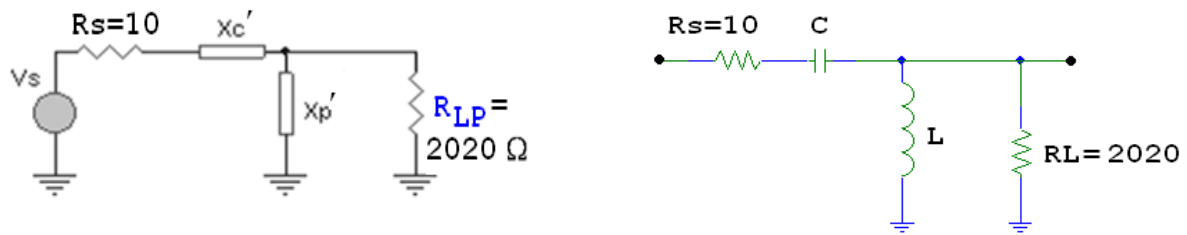


$$Q_S = Q_P = \sqrt{\frac{R_P}{R_S} - 1} = \sqrt{\frac{2020}{10} - 1} = 14,177$$

$$Q_S = \frac{X_S}{R_S} \quad \text{sehingga} \quad X_S = Q_S \times R_S = 14,177 \times 10 = 141,77\Omega$$

Karena bersifat HPF, X_S berupa C sehingga $X_S = -j 141,77\Omega$


$$Q_P = \frac{R_P}{X_P} \quad \text{sehingga} \quad X_P = \frac{R_P}{Q_P} = \frac{2020}{14,177} = 142,48\Omega$$

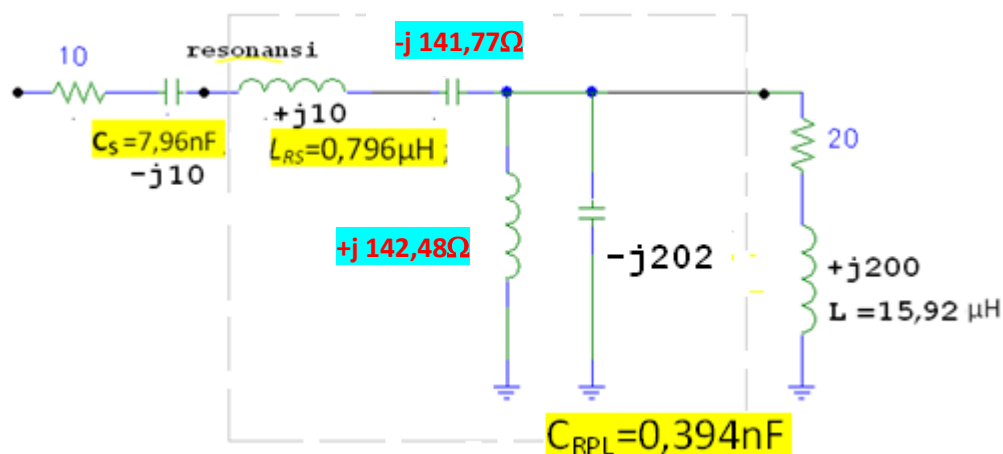Karena bersifat HPF, X_P berupa L sehingga $X_P = +j 142,48\Omega$




Komponen akhir pada rangkaian adalah sbb:

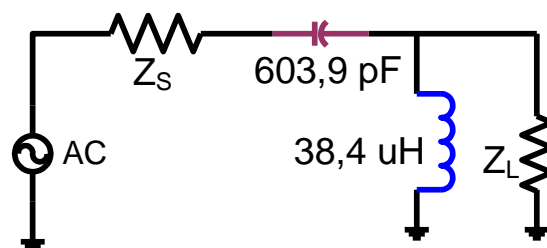- X_S akhir = $+j 10 \Omega$ seri dengan $-j141,77 \Omega = -j 131,77\Omega$ berupa kapasitor $C = 603,9 \text{ pF}$
- X_S akhir = $-j 202 \Omega$ paralel dengan $+j142,48 \Omega = \frac{(j142,48) \times (-j202)}{(j142,48) + (-j202)} = +j 483,55\Omega$ berupa Induktor $L = 38,4 \mu\text{H}$



b)Metoda Absorpsi :

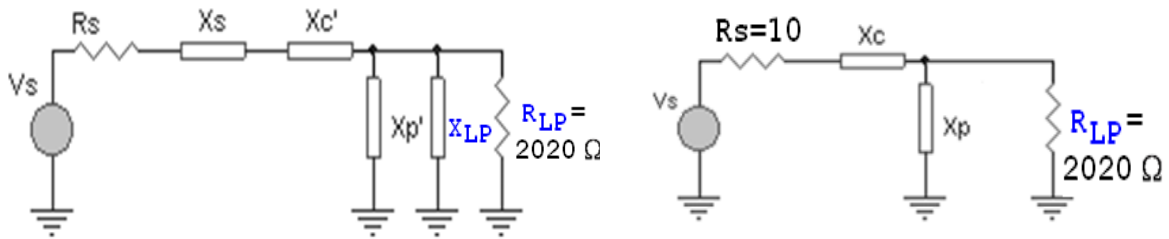

$$Q_S = Q_P = \sqrt{\frac{R_P}{R_S} - 1} = \sqrt{\frac{2020}{10} - 1} = 14,177$$

$$Q_S = \frac{X_S}{R_S} \text{ sehingga } X_S = Q_S \times R_S = 14,177 \times 10 = 141,77\Omega$$

Karena bersifat HPF, X_S berupa C sehingga $X_S = -j 141,77\Omega$

$$X_S = -j 141,77\Omega = -j 10 + X_{\text{solusi}} \rightarrow X_{\text{solusi}} = -j 131,77\Omega \rightarrow C = 603,9\text{pF}$$

$$Q_P = \frac{R_P}{X_P} \text{ sehingga } X_P = \frac{R_P}{Q_P} = \frac{2020}{14,177} = 142,48\Omega$$

Karena bersifat HPF, X_P berupa L sehingga $X_P = +j 142,48\Omega$

$$X_P = +j 142,48\Omega = +j202 // X_{\text{solusi}}$$

$$\frac{1}{X_P} = \frac{1}{j142,48} = \frac{1}{+j202} + \frac{1}{X_{\text{solusi}}} \Rightarrow \frac{1}{X_{\text{solusi}}} = \frac{1}{j142,48} - \frac{1}{+j202}$$

$$\Rightarrow \frac{1}{X_{\text{solusi}}} = \frac{1}{j142,48} + \frac{1}{-j202} = j142,48 \text{ paralel} - j202 = +j 483,55$$

$$\Rightarrow L = 38,4 \mu\text{H}$$

Rangkaian menjadi :

